
STEVAL-ILD004V1: leading-edge dimmer

Introduction

The purpose of this board is to propose an innovative and low cost power topology using two sensitive SCRs and a single IGBT to dim all kind of lamps: 100 - 240 V halogen lamps, SELV halogen lamps through magnetic or electronic transformers, and the new CFL and LED dimmable lamps.

The main features of this dimmer are:

- Operation for 2-wire wall dimmer
- Leading-edge control only (compatible with all lamps commonly found on the shelves)
- Operation on 110 V or 230 V line rms voltage and 50 Hz or 60 Hz line frequency
- Dimmable power range (note: higher power is possible with larger heatsink):
 - 3 to 600 W for 230 V rms line
 - 3 to 300 W for 110 V rms line
 - power efficiency @ 230 V > 99%
 - standby losses @ 230 V < 0.3 W
- Short-circuit protection at startup
- Enhanced interface with pushbuttons; soft-start and soft-stop; memory of last setting
- Compliance with EMC standards:
 - Compliant with EN55015 (for European market)
 - Criteria A for 2 kV IEC 61000-4-5 surge for fast transients above 2.5 kV according to IEC 61000-4-4)

This document describes the principle and operating conditions of this demonstration board. The performance of this board is described regarding power losses and EMC standard test results. The description of the user interface and connections will help users to setup and evaluate this dimmer.

Figure 1. STEVAL-ILD004V1 board



Contents


Contents	2
1 Operation principle and targeted application	4
1.1 Dimmer for CFL, LED and halogen lamps	4
1.2 Operation principle	4
1.3 Selected components	5
1.3.1 Silicon controlled rectifier (SCR)	5
1.3.2 IGBT	5
1.3.3 Microcontroller unit (MCU)	6
1.4 Operating conditions	6
2 Board performances	7
2.1 Soft-start and soft-stop	7
2.2 CFL and LED operation	7
2.3 Conducted noise	8
2.4 Short-circuit protection	8
2.5 Immunity	9
2.6 Power losses	10
2.7 Standby losses	11
2.8 Voltage surges	12
3 Getting started	13
3.1 Board connection and options	13
3.2 User interface	14
3.3 Safety instruction	14
3.4 Test procedure and test points	15
3.5 Possible changes	15
3.6 Issue solving	16
4 Conclusion	17
Appendix A Dimmer schematic	18

Appendix B	Board layout and silkscreen.....	19
Appendix C	Bill of materials	20
Appendix D	Dimmer phase angle table	22
Appendix E	Power losses and temperatures for a 300 W, 110 V load.....	23
Appendix F	Heatsink design exemple ($R_{th} = 11\text{ °C/W}$)	24
Appendix G	Dimmer schematic without IGBT (L-C filter values given for 300 W - 120 V dimmer).....	25
Revision history		26

The switch command sequence is shown on [Figure 3](#).

The IGBT is first switched on to control the current rising edge. After 300 μ s, the SCR is switched on to reduce the on-state forward voltage drop of the dimmer and then the conduction power losses are decreased. A 2.2 μ H inductor (L), is added in series with both SCRs to slow down the current variation due to this voltage drop dip which occurs when the current switches from the IGBT to the SCR.

Figure 3. Switch command sequence (500 W, 230 V Halogen lamp)

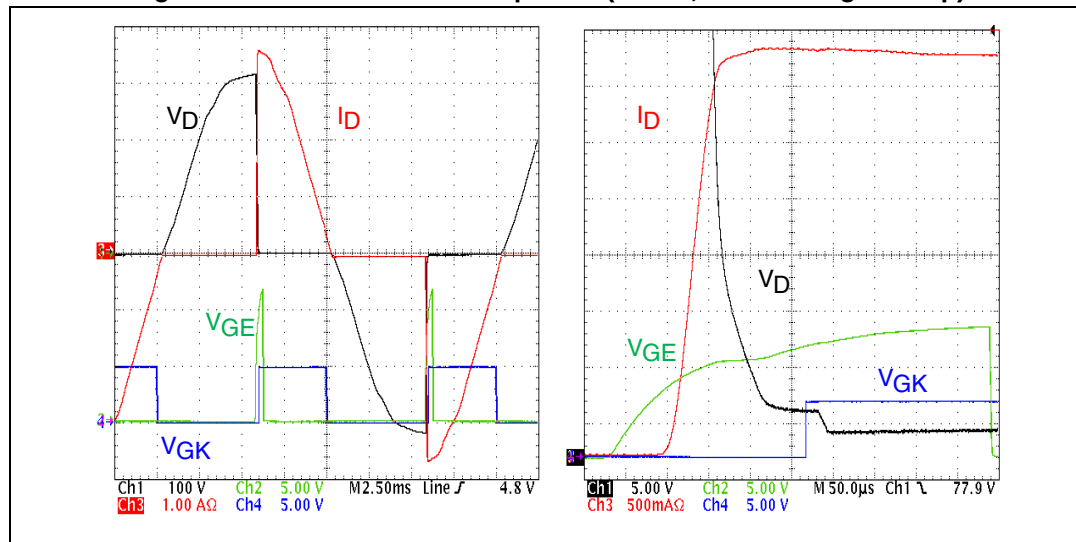

1.3 Selected components

1.3.1 Silicon controlled rectifier (SCR)

One of the main characteristics of the SCR for this application is its low gate current. TS820-600FP features a maximum I_{GT} of 200 μ A. Using the TO220 full pack insulated package ensures just one heatsink can be used for both SCRs.

TS820-600FP main characteristics are:

- On-state rms current, $I_{T(RMS)} = 8$ A up to a 91°C case temperature.
- Repetitive peak off-state voltage, $V_{DRM}/V_{RRM} = 600$ V.
- Non repetitive surge peak on-state current for a 10 ms pulse, $I_{TSM} = 70$ A

1.3.2 IGBT

A 10 A 600 V IGBT, the STGF10NC60KD, is used for current commutations. This IGBT is also in full pack to have the same non-insulating heatsink for this IGBT and the two SCRs.

STGF10NC60KD main features are:

- Lower on voltage drop, $V_{CE(sat)} = 1.8$ V typ. For $I_C = 5$ A and $T_j = 125$ °C
- Lower C_{RES} / C_{IES} ratio for better noise immunity
- Short-circuit time up to 10 μ s supported.

1.3.3 Microcontroller unit (MCU)

The STM8S103F2 has been chosen as it fits very well with the light dimmer application requirements. Its main features are:

- 16 MHz advanced STM8 core with Harvard architecture and 3-stage pipeline
- Program memory: 8 Kbyte Flash
- Data memory: 640 bytes true data EEPROM
- RAM: 1 Kbyte
- Up to 17 I/Os on a TSSOP 20-pin package including 12 high sink outputs
- 16-bit general purpose timer, with 3 CAPCOM channels (IC, OC or PWM)
- 8-bit basic timer with 8-bit pre-scaler

1.4 Operating conditions

This board is designed to drive all kind of lamps for a wide range of applications:

- Power mains:
 - rms voltage ($\pm 10\%$): 100 - 120 V or 220 - 240 V
 - Frequency: 50 Hz or 60 Hz
 - Ambient temperature: 0 °C to 60 °C (closed box operation allowed, refer to [Section 2.6](#))
- Supported loads:
 - Power range: from 3 W to 600 W, for a 230 V rms mains voltage (300 W max for 110 V)
 - Dimmable compact fluorescent lamps
 - Dimmable LED lamps
 - Incandescent lamps
 - Halogen lamps
 - Electronic dimmable transformers
 - Magnetic transformers

2 Board performances

2.1 Soft-start and soft-stop

For an enhanced smart control, a soft-start and a soft-stop are implemented in software. This means that, at the dimmer power-on or power-off respectively, the light increases until the last set power level (or 50% in case of 1st utilization) or decreases until lamp light off. This on/off control is activated when the on/off pushbutton is pressed more than 100 ms.

Dimmer soft-start (or soft-stop) consists of automatically setting up every turn-on angle in the register table to the previously set value. Each step is set during 200 ms. For example, at the first dimmer plug-in, 7 steps are needed to reach the mid-power. The soft-start lasts then 1.4 second.

Programmed dimmer phase angle list is given in [Appendix D](#) for 50 and 60 Hz line frequencies.

2.2 CFL and LED operation


For low consumption lamps, the main issue of dimmers today is the required minimum current to keep the power switch on and to avoid lamp flickering.

Thanks to the DC gate control of the TS820, the lamp current can reach zero and the SCR remains latched as previously explained. An example is shown [Figure 4](#) with an 8 W dimmable LED lamp, where the lamp current clearly goes to zero without causing any issue.

The use of SCR for the current conduction, contrary to MOS-gate device, allows good operation with inductive loads and also in case several lamps are used in parallel.

The board can dim lamps between 36° to 144° (which is equivalent to 2 ms to 8 ms for a 50 Hz line frequency, see [Appendix D](#)) of the mains cycle. That induces a light brightness variation from 5 to 90% of the nominal power of the lamp.

Figure 4. 8 W LED lamp dimming

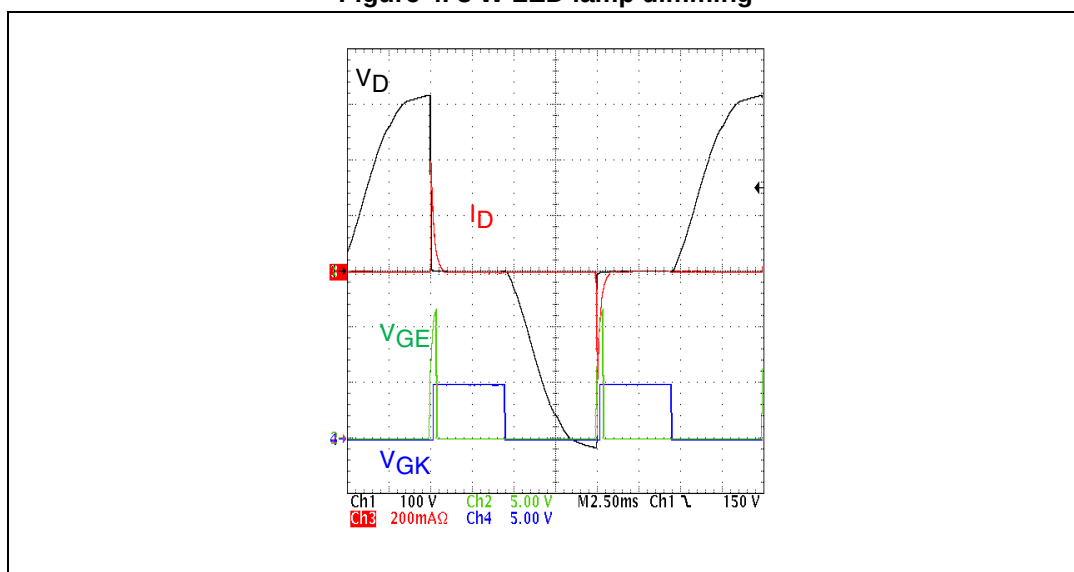


2.3 Conducted noise

EMC directives have to be fulfilled for appliances sold in the European market. This dimmer has then in particular to fulfill the EN55015 standard. This standard defines the maximum levels of the conducted noise due to mains current switching.

To limit this noise, the IGBT gate circuit (refer to R3 and C16 in board schematic on [Appendix A](#)) is designed to reduce the rising edge of the mains current.

[Figure 5](#) illustrates the EMI noise measured according to EN55015, for the maximum switched current, i.e. for the maximum load power (a 600 W / 230 V halogen lamp) dimmed at a 5.5 ms turn-on angle (50 Hz line frequency).

Figure 5. EN55015 standard validation (600 W – 230 V halogen lamp dimmed at 5.5 ms)

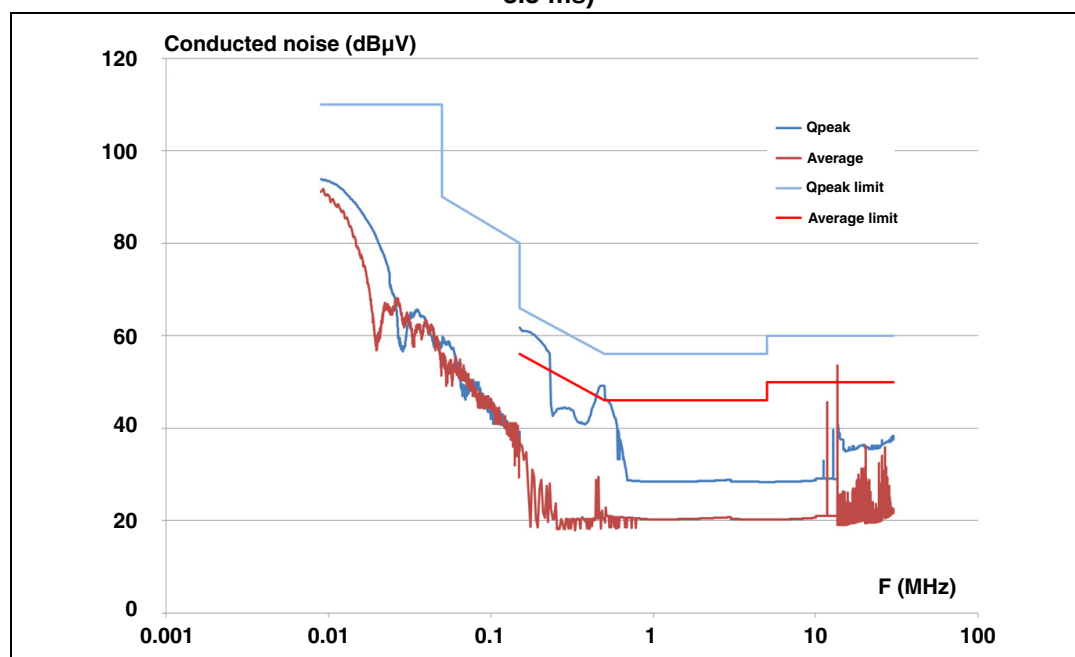

2.4 Short-circuit protection

To avoid adding a fuse (and then cause any issue in case the end user has to replace it), the board is self protected against a short-circuit event. This can occur if the dimmer is wrongly connected.


The protection is achieved with a shunt resistor (R22) used to detect an overcurrent. A hardware protection, with transistors Q11 and Q12, is implemented to turn off the IGBT quickly. The short-circuit information is also sent to the MCU through PA1 I/O port.

In case of a short-circuit detection, the MCU does not turn the SCRs on. An IGBT turn-on trial is performed at the next half cycle. If the current detected by R22 is still above the defined limit (here 12.5 A, as it is the current required to reach 0.6 V through the 0.047 ohm R22 resistor), and if this happens for four consecutive trials, the board is then definitely turned off. A green LED (D5) informs the user that a short-circuit has been detected. The only way to restart the board is to disconnect it from the power mains and plug it back after few minutes.

Figure 6 shows the overcurrent protection in the case of triggering at peak line voltage on a short-circuited load, with a 264 V mains rms voltage (i.e. 240 V + 10%). It should be noted that, thanks to the soft-start procedure, the initial turn-on normally occurs only for a 170° turn-on delay. This means that the voltage across the dimmer should be below 50 V instead of 380 V as on the test shown on Figure 6. The IGBT thermal stress is then greatly reduced in normal short-circuit operation.

Note that a load short-circuit occurs usually in case of mistaken connection. This means that the overcurrent protection will work at first turn-on, i.e. for a 170° turn-on delay. In case of lamp flash-over (which can occur at the end of life of incandescent lamps) the short-circuit occurs during dimmer conduction. The SCRs are then on and will sustain the flash-over current. Indeed this current is equivalent to a mains short-circuit (so typically around 250 A peak) but lasts typically only 1 ms. The current stress is thus equivalent to 31 A².s which is well below the specified I²t of the TS820 (45 A².s).

Figure 6. Short-circuit overcurrent protection behavior

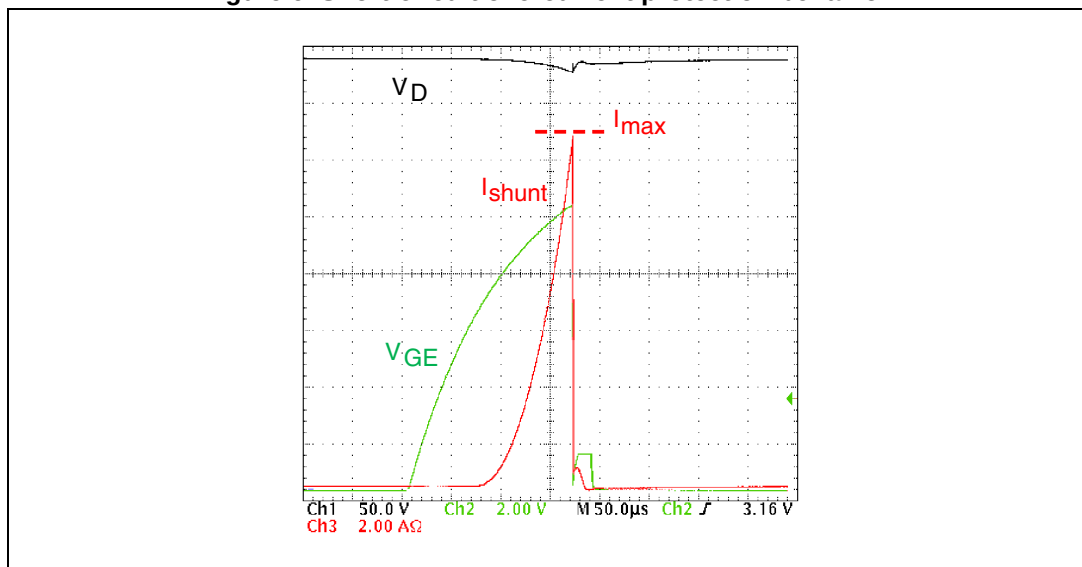


2.5 Immunity

At board plug-in, a fast voltage transient can be applied to the semiconductor switch and can exceed the SCR dV/dt capability. This is not a major issue for an SCR that will then turn on safely and will not be damaged as long as the load current is below the SCR maximum current capability.

To avoid the SCR turn-on, sensitive SCR dV/dt support can be greatly improved when its gate is short-circuited to its cathode. For this purpose, a normally on N-MOS is connected between each SCR gate and cathode terminals (refer to Q13 and Q14 on Figure 7). These MOS devices are turned off thanks to C17 which charges both N-MOS gates to a negative voltage when PA03 I/O pin is pulled down to zero.

Figure 7. SCR gate circuit for dV/dt withstanding improvement

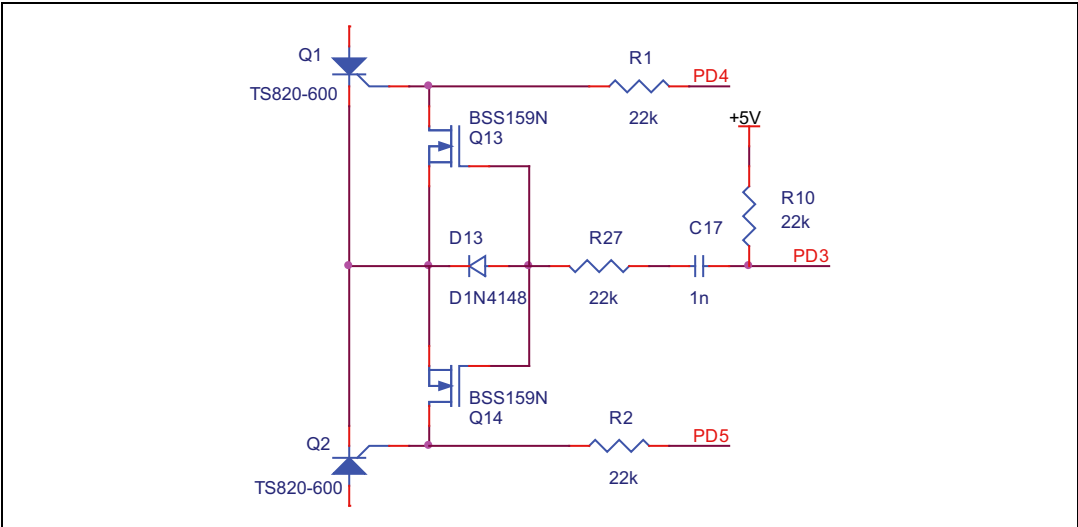

This gate circuit also helps to withstand fast transient voltages as described in the IEC 61000-4-4 standard. The X2 capacitor and a specific reset software routine (which allows previous configuration restoration - on or off status, set power level) allow high levels to be supported. [Table 1](#) gives the board minimum supported levels according to the IEC 61000-4-4 test conditions, for the different coupling modes.

Table 1. IEC61000-4-4 board minimum level supported levels

Line coupling	L		N	
Burst polarities	+	-	+	-
5 kHz	4 kV	3.3 kV	2.7 kV	3.2 kV
100 kHz	3 kV	2.7 kV	2.6 kV	2.8 kV

IEC 61000-4-4 test conditions are:

- Load is a 50 W, 230 V halogen lamp
- The minimum withstood burst level (given in [Table 1](#) is the maximum burst voltage, applied for 1 minute, without any lamp light on)
- Mains voltage is 230 V rms / 50 Hz
- 5 kHz or 100 kHz burst frequency
- Board at 10 cm from the reference plane


The dimmer is able to withstand up to 2.6 kV for the worst case which is above the 2 kV required by the standard for home appliances.

2.6 Power losses

Total power losses are split into IGBT turn-on switching losses and SCR conduction losses.

[Figure 8](#) shows the different power losses measured with a 600 W, 230 V halogen lamp, which is the worst case, and with the IGBT gate circuit which allows EN55015 to be fulfilled as shown on [Figure 5](#).

Figure 8. Power losses for a 600 W, 230 V halogen lamp

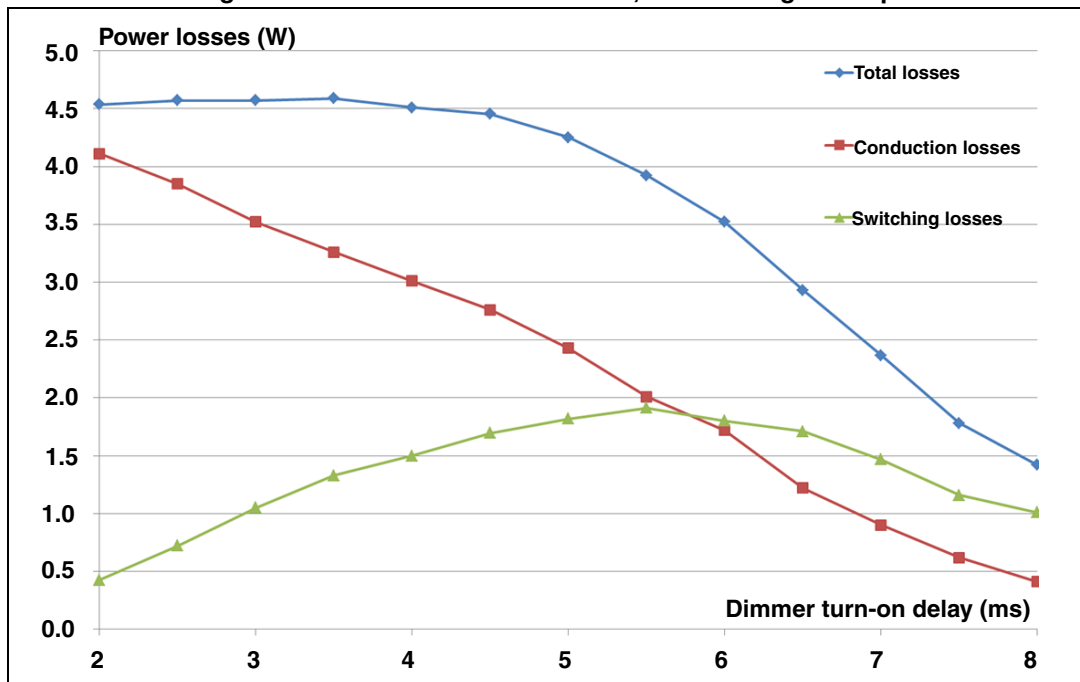

Maximum power losses are reached for the maximum conduction time and are lower than 4.5 W. We have performed tests in a closed box environment with limited heat transfer capability. Then, as the heatsink is put vertically (as it is traditionally mounted in a wall dimmer application), its aluminum heatsink (maximum length: 58 mm; area: 3076 mm²; thickness: 1 mm) presents an 11 °C/W thermal resistor (refer to [Appendix F](#)).

The heatsink maximum temperature, in steady state (i.e. after more than 8 hours of continuous operation), reaches 108 °C for the maximum conduction time. This gives a maximum junction temperature of respectively 113 °C for the TS820 and lower than 111 °C for the STGF10NC60KD. The maximum average ambient temperature is then slightly higher than 60 °C (67 °C is measured inside the box at the top, whereas 57 °C is measured at the bottom).

Values measured for a 110 V rms line voltage are given in [Appendix E](#).

2.7 Standby losses

Standby losses are mainly due to the MCU consumption. For the STM8S103F2, using the halt mode (low consumption MCU mode) the maximum current consumption at 125°C is 105 µA (cf SMT8S datasheet).

The quiescent current of the 5 V voltage regulator (U2) has also to be taken into account (typically 100 µA).

The dimmer standby losses, for a 0.2 mA power supply output current, is 0.29 W at 230 V rms.

Note: This dimmer is not concerned under standby directives as the board does not feature any display or any sensor to automatically exit from the standby mode (the “wake-up” is initiated by the end-users when they push a button).

2.8 Voltage surges

Thanks to a S20K250 varistor (RV1), the board is immune against voltage surges up to 2 kV when the dimmer is in the off-state.

When the dimmer is in the on-state, the SCR features a high current capability which makes it able to withstand a surge current coming from a 2 kV surge, as described in the IEC 61000-4-5 standard.


Following figures show the dimmer behavior in case of voltage surges.

For this test, a 2 kV voltage surge is applied on the peak mains voltage. The dimmer is placed in series with a 600 W - 230 V halogen lamp.

For [Figure 9](#), left-side, the dimmer is in OFF-state. The 2 kV surge energy is absorbed by the varistor which clamps the dimmer voltage to 600 V (equal to maximum non repetitive surge off-state voltage allowed for the SCR and the IGBT).

On the second case, the dimmer is in ON-state when the 2 kV voltage surge is applied. Thanks to the high over-current capability of the TS820-600FP, the 8/20 μ s current surge is absorbed by the SCR without any damage, even after have applied 10 times 2 kV positive surges and 10 times 2 kV negative positive.

Figure 9. IEC 61000-4-5 board performance

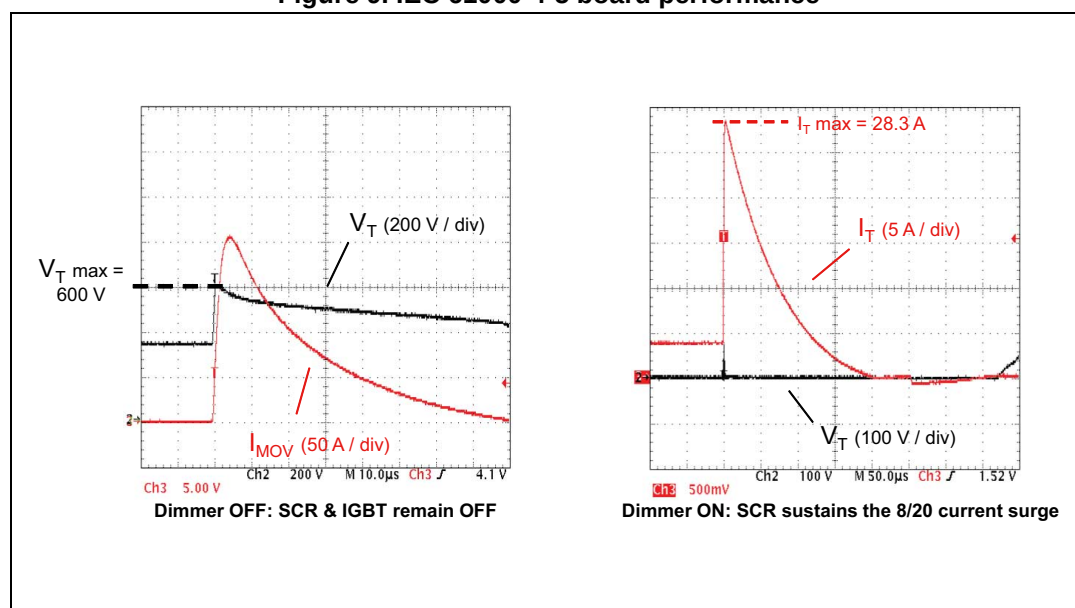


3 Getting started

3.1 Board connection and options

Figure 10 shows the connection diagram of the board (please refer to [Section 3.3](#) before performing any test):

- Header J1 is used to connect the dimmer to the mains in series with the lamp
 - Terminals T1 or T2 can either be connected to the load or directly to the mains.
 - Appropriate connection of the lamp, to mains neutral or line, will depend on electrical safety regulations. Usually the lamp has to be connected to neutral.
- J2 connector is a 4-pin connector used to connect an MCU programmer (example: STM8S Discovery Kit) for software upload, or inboard debugging.
- Several straps allow the user to add some optional components:
 - Strap 1: this strap can be used to add a thermal fuse.
 - Strap 2: this strap can be replaced by an inductor in case an EMI passive filter is preferred to an IGBT. IGBT Q3 has then to be disconnected by removing strap 3 for EMI evaluation and C15 input capacitor should be increased especially if compliance to EN55105 is expected.
 - Strap 3: this must be removed to disconnect the IGBT as explained just above.

Figure 10. Board connection diagram

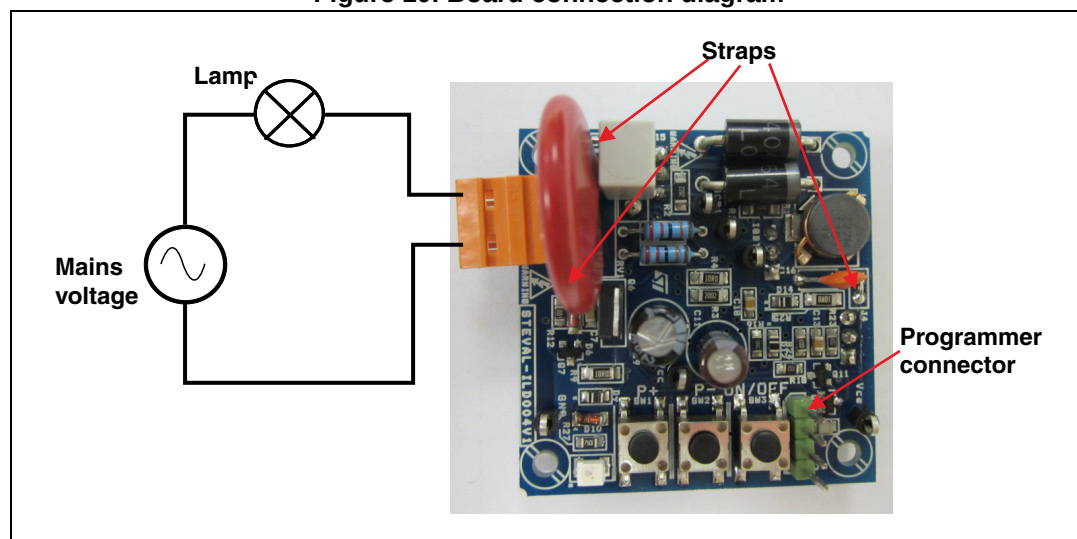


3.2 User interface

Figure 11 shows user interface pushbuttons and measurement points:

- **ON/OFF** pushbutton: this button is used to turn on or turn off the dimmer.
- **P+** pushbutton: a short pressure (> 100 ms for 50 Hz operation) on this button produces an increase of lamp light of one step. A longer pressure allows changing the power level continuously.
- **P-** pushbutton: a short pressure (> 100 ms for 50 Hz operation) on this button produces a decrease of lamp light of one step. A longer pressure allows changing the power level continuously.
- **SC LED**: when on, this LED indicates that a short-circuit has been detected four times consecutively. The whole board will remain off up to line disconnection and plug back.

Figure 11. User interface and test points (in blue)

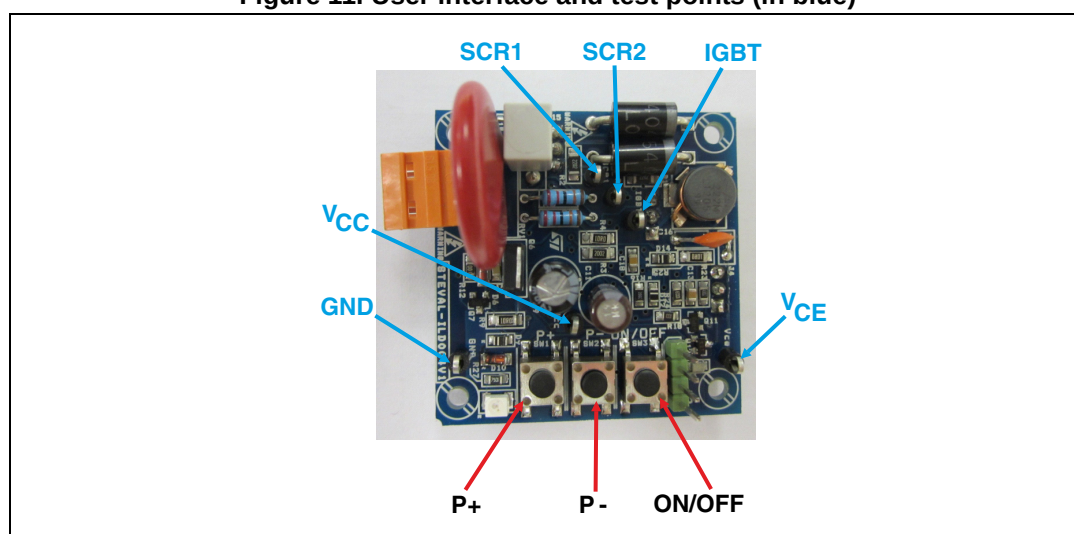

3.3 Safety instruction

Warning: The high voltage levels used to operate the SCR dimmer evaluation board could present a serious electrical shock hazard. This evaluation board must be used in a suitable laboratory by qualified personnel only, familiar with the installation, use, and maintenance of electrical power systems.

The STEVAL-ILD004V1 evaluation board is designed for demonstration purposes only, and shall not be used either for domestic installation or for industrial installation.

3.4 Test procedure and test points

Follow this procedure to use the STEVAL-ILD004V1 board:

1. Connect one lamp terminal to one of J1 header terminal (T1 or T2) as shown on [Figure 10](#).
2. Connect the other lamp terminal and the other J1 terminal to a powered off mains plug.
3. Put the mains voltage on.
4. Press the on button to switch the lamp on. Take care to use a non-conductive tool to press each pushbutton to avoid any contact with live parts which are under line voltage.
5. Press P+ and P- buttons, always with a non-conductive tool, to change the lamp brightness.

Using certain connectors ([Figure 11](#)), it is possible to measure several electrical signals:

- IGBT = IGBT gate command (MCU output)
- SCR1 and SCR2: respectively Q1 and Q2 gate commands (MCU output)
- V_{CE} = IGBT collector terminal, to measure collector-emitter voltage if voltage probe is connected to GND
- V_{CC} = DC power supply voltage for IGBT gate drive (12 V)
- GND: board control reference; all previous voltages must be measured referenced to this GND connector

Please note that the STEVAL-ILD004V1 board is not insulated from the mains voltage. All test or measurement equipment has then to be insulated from the mains to avoid line short-circuit though this equipment ground circuit. Also as soon as a measurement ground is connected to the board, the equipment ground can be connected to the line voltage and could cause user electrical shock if proper test procedures are not applied.

3.5 Possible changes

The following changes can be applied by the end user if needed:

- Implement an EMI filter instead of IGBT for EMC conducted noise fulfillment. The board schematic of such a dimmer will then be greatly simplified (refer to [Appendix G](#)). To evaluate this solution, you have to follow this procedure: Using strap 2, an inductor can be added and the C15 X2 capacitor can be changed. For example, for 300 W US dimmer a 29 μ H inductor and a 100 nF capacitor can be used. For a 500 W European dimmer, a 2.4 mH inductor and a 100 nF capacitor can be used to fulfill EN55015 standard. Strap 3 must be removed in this case to disconnect the IGBT collector.
- IGBT gate resistor, used to control the turn-on speed (R3), can be changed for a different losses/noise trade-off. This can be done if a different load power than 600 W, 230 V is targeted or if EN55015 has not to be fulfilled.

If J2 connector is used to upload the MCU software, the board has to be disconnected from the mains before connecting the programmer.

3.6 Issue solving

If the LED is lit and if the board does not answer to pushbutton pressure, this means a short-circuit has been detected. You need to restart the dimmer. Disconnect it from the mains, wait few minutes to let the V_{DD} level (5 V) decrease below at least 2.5 V, and reconnect it with a new load before restarting the dimmer.

4 Conclusion


The STEVAL-ILD004V1 demonstration board allow designers to implement a leading-edge light dimmer which will be directly compliant with market requirements.

These requirements are:

- Dim all kind of dimmable lamps without any problem:
 - From 3 to 600 W, 230 V power loads (or 300 W for 110 V)
 - Halogen, CFL, LED and transformer (magnetic or electronic)
- Compliant with European EMC standards:
 - EN55015: Limits and methods of measurement of radio disturbance characteristics of electrical lighting and similar equipment
 - IEC61000-4-4: Testing and measurement techniques – electrical fast transient/burst immunity test
 - IEC61000-4-5: Testing and measurement techniques – surge immunity test
- Smart interface:
 - Soft-start and soft-stop
 - Setting memory
 - Protection against load short-circuit due to connection error

Appendix A Dimmer schematic

Figure 12. Dimmer schematic

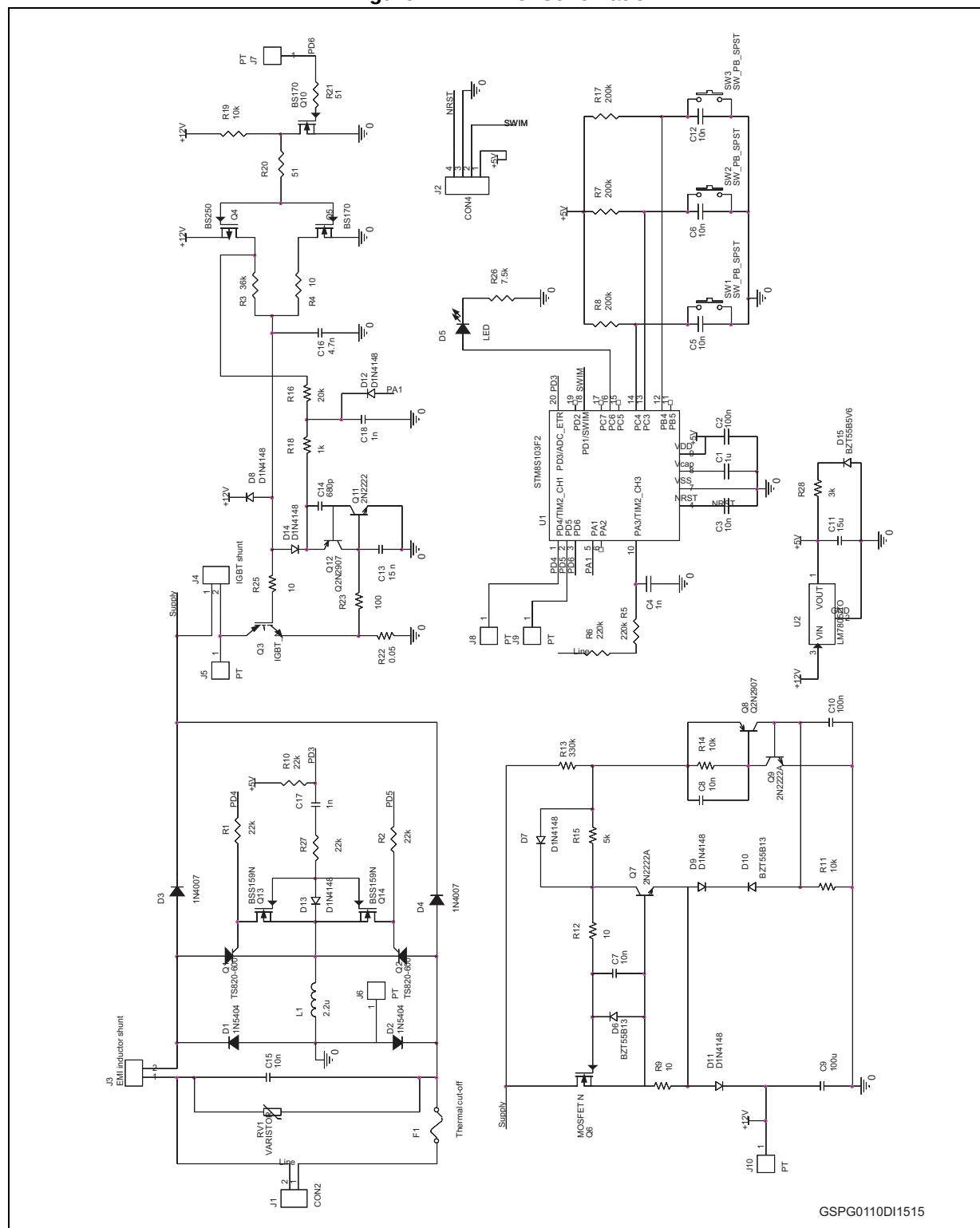

Appendix B Board layout and silkscreen

Figure 13. Component layout


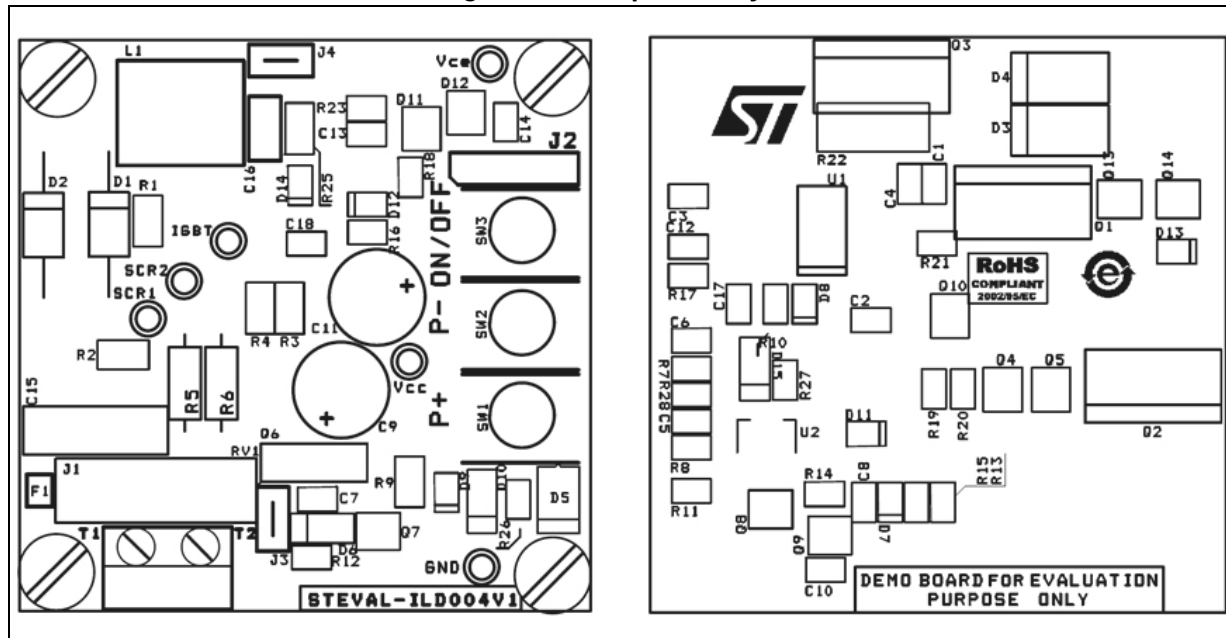


Figure 14. Board layout

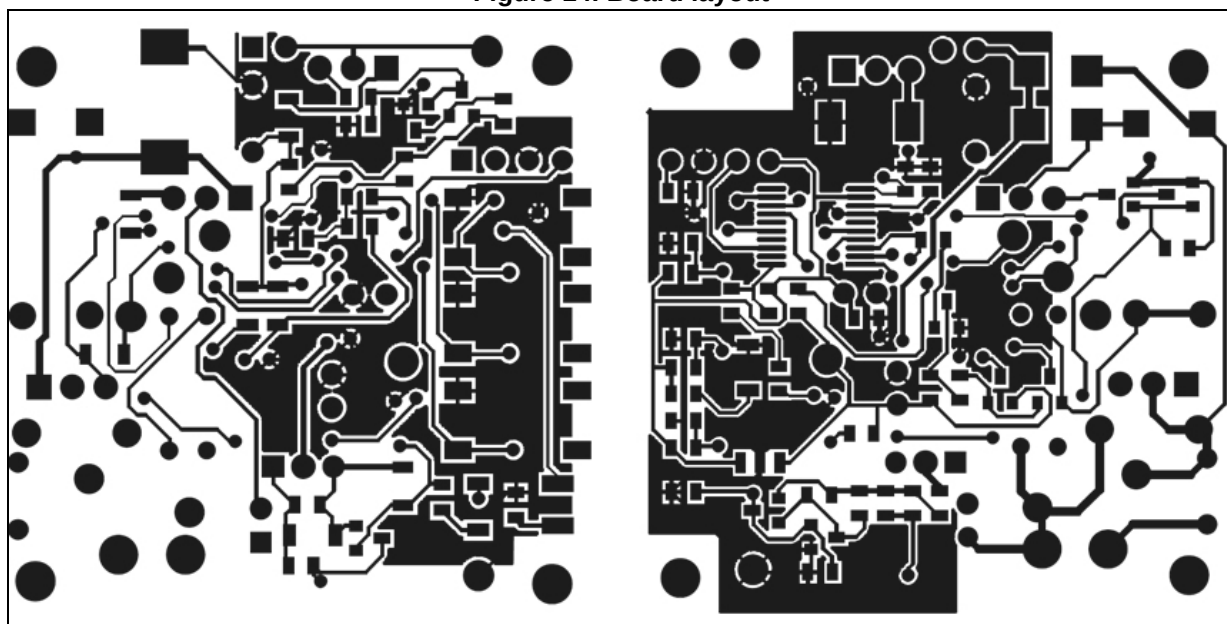

Appendix C Bill of materials

Table 2. Bill of material (BOM)

Reference	Part
C1	1u
C2,C10	100n
C3,C5,C6,C7,C8,C12	10n
C4,C17,C18	1n
C9	100u / 25V
C11	15u / 63V
C13	15 n
C14	680p
C15	10n
C16	4.7n / 63 V
D1,D2	1N5404
D3,D4	MRA4007
D6	BZV55C15
D7,D8,D9,D11,D12,D13,D14	D1N4148
D15	5,6V zener diode
D10	BZT55B13
D5	LED
F1	Thermal cut-off shunt
J1	CON2
J2	CON4
J3	EMI inductor shunt
J4	IGBT shunt
J5,J6,J7,J8,J9,J10	PT
L1	2.2u
Q1,Q2	TS820-600FP
Q3	STGF10NC60KD
Q4	BS250
Q5,Q10	BS170
Q6	MOSFET N / STD1NK60
Q7,Q9,Q11	2N2222A/ZTX
Q8,Q12	Q2N2907
Q13,Q14	BSS159N

Table 2. Bill of material (BOM) (continued)

Reference	Part
RV1	VARISTOR S20K250
R1,R2,R10,R27	22k
R3	36k
R16	20k
R4,R12,R25	10 Ohm
R5,R6	220k / 350 V / 0.6W
R7,R8,R17	200k
R9	1 Ohm
R11,R14,R19	10k
R13	330k
R15	5k
R18	1k
R20,21	51 Ohm
R22	0.05 Ohm / 0.5 W
R23	100
R26	7.5k
R28	3k
SW1,SW2,SW3	SW_PB_SPST
U1	STM8S103F2
U2	LD2981ABU50

Appendix D Dimmer phase angle table


Table 3. Dimmer phase angles

Angle number	Angle (°)	50 Hz delay (ms)	60 Hz delay (ms)
1	36	2	1.7
2	45	2.5	2.2
3	54	3	2.6
4	63	3.5	3.0
5	72	4	3.5
6	81	4.5	3.9
7	90	5	4.3
8	99	5.5	4.8
9	108	6	5.2
10	117	6.5	5.6
11	126	7	6.1
12	135	7.5	6.5
13	144	8	6.9

Appendix E Power losses and temperatures for a 300 W, 110 V load

Figure 15 shows the different power losses measured with a 300 W, 110 V halogen lamp, with the same IGBT gate circuit designed to fulfill EN55015 standard (see [Section 2.3: Conducted noise](#)).

Figure 15. Power losses for a 300 W, 110 V halogen lamp

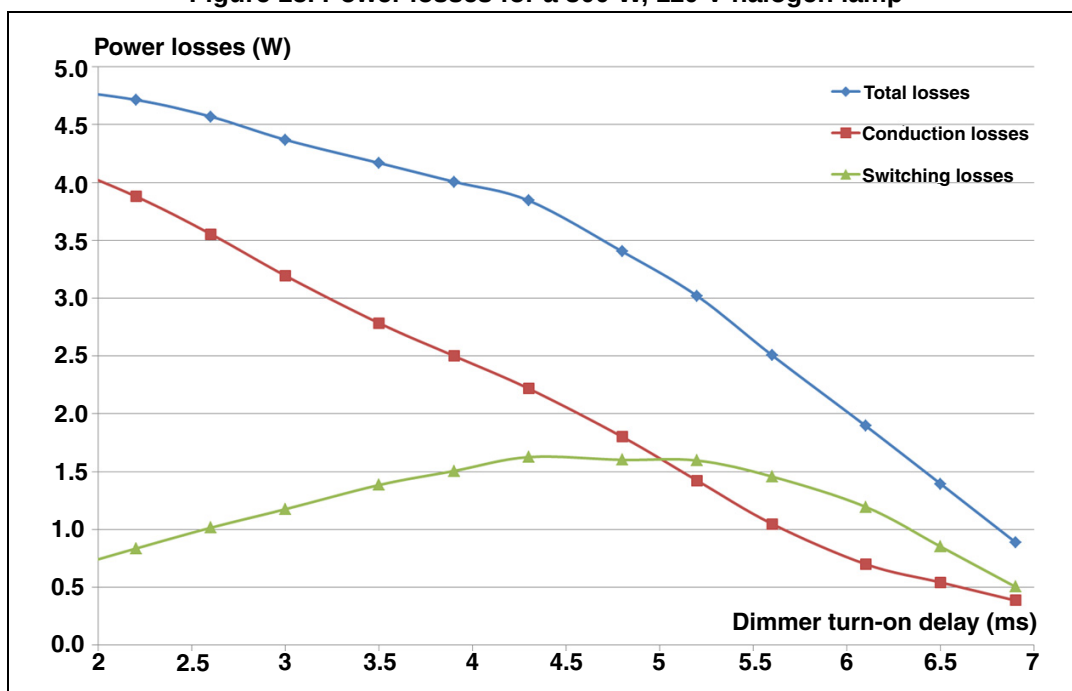

Maximum power losses are reached for the maximum conduction time and are equal to 4.7 W. These power losses are then slightly higher than those measured for the 600 W, 230 V load (4.5 W). Tests similar to those in [Section 2.6: Power losses](#) could be performed in a closed box environment. The junction temperatures of both the SCR and the IGBT will here again remain below the maximum allowed limits.


It should be noted that for the North American market, compliance to EN55015 is not mandatory. Then the IGBT gate resistance (R3) or capacitor (C16) could be reduced to reduce the switching losses. It should be noted that setting these values to a too low value could produce acoustic noise due to the mechanical oscillations of the tungsten lamp filaments.

Appendix F Heatsink design exemple ($R_{th} = 11 \text{ }^{\circ}\text{C/W}$)

Figure 16 gives the package outline of the heatsink used in our STEVAL-ILD004V1 board. The heatsink made with a 1 mm thick aluminium plate. Its thermal resistor is typically 11 $^{\circ}\text{C/W}$.


Figure 16 dimensions are give in millimeters.

Figure 16. Heatsink design exemple

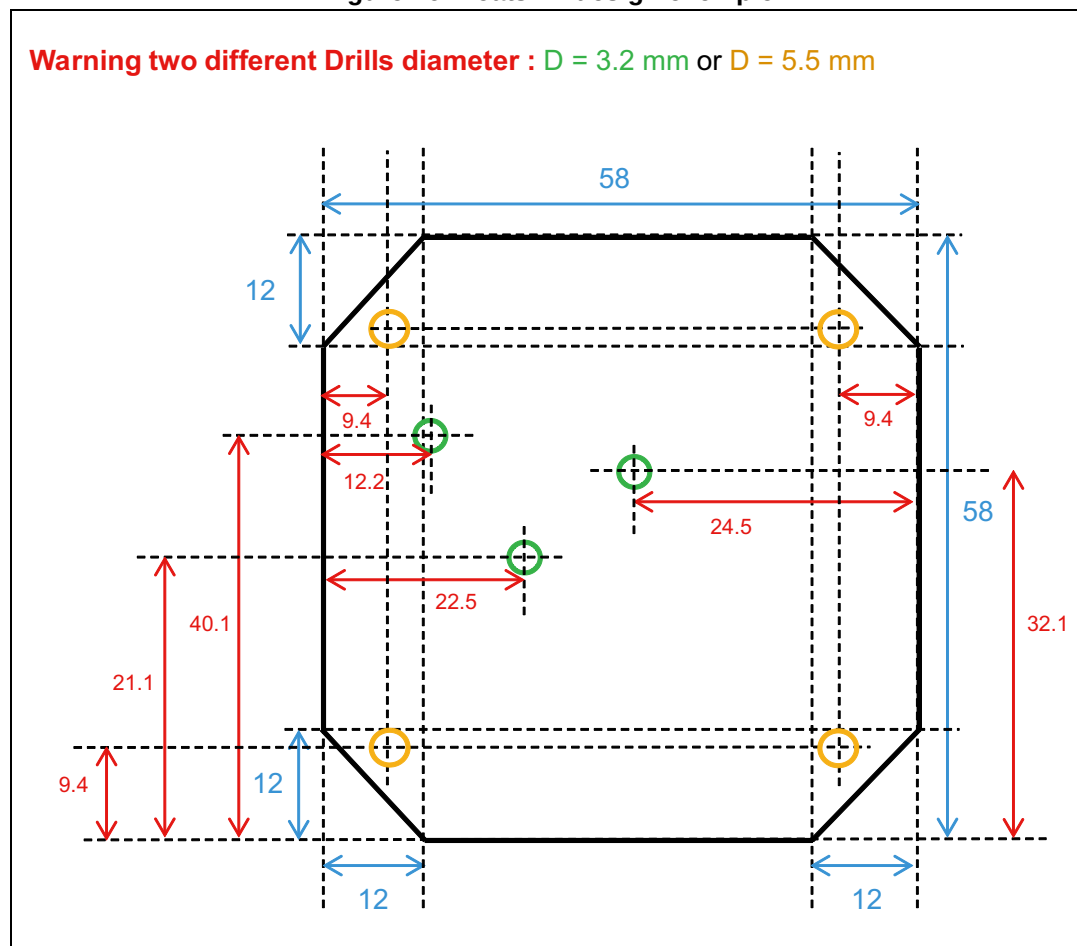

Appendix G Dimmer schematic without IGBT (L-C filter values given for 300 W - 120 V dimmer)

Figure 17. Dimmer schematic

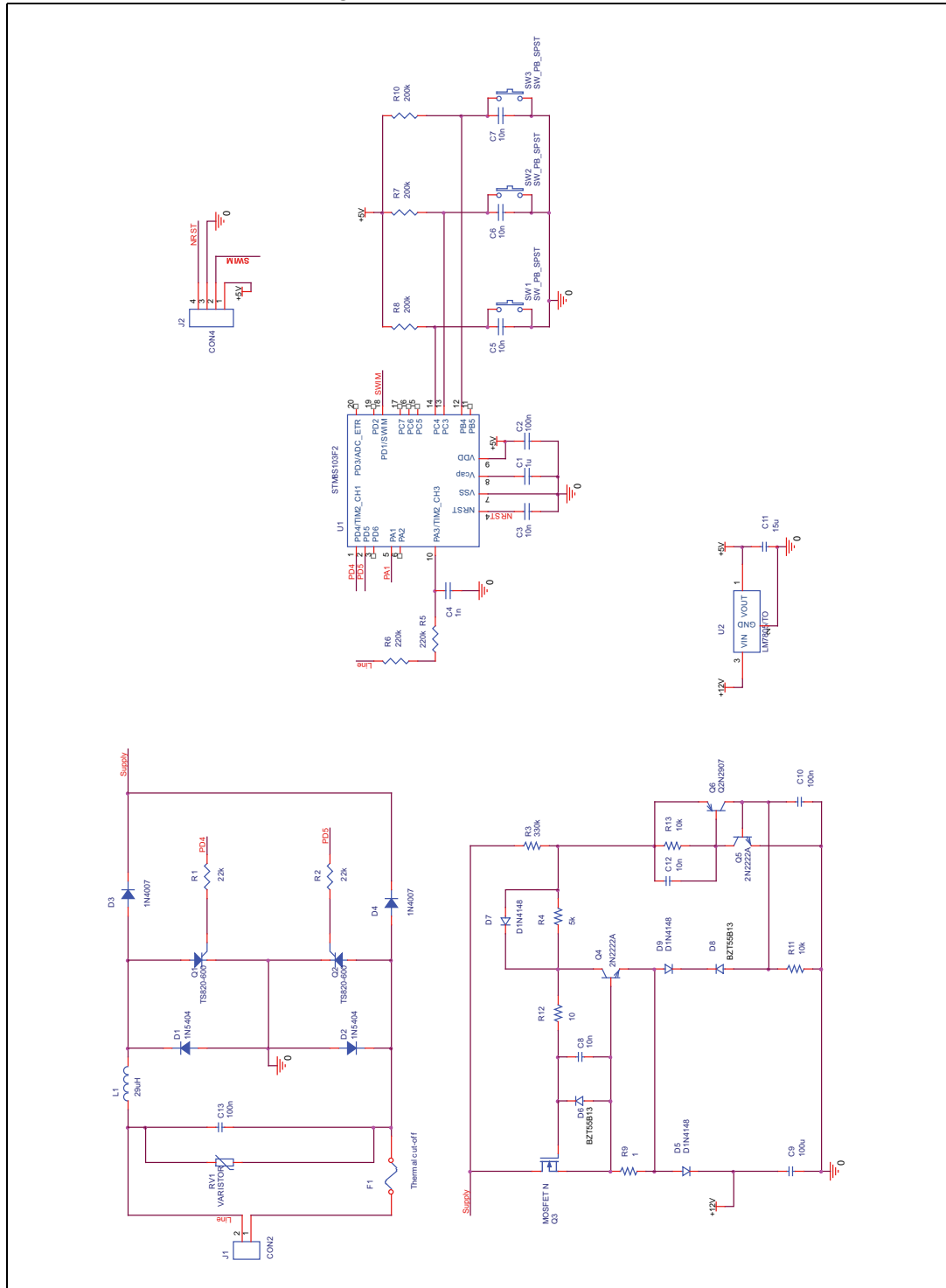

Revision history

Table 4. Document revision history

Date	Revision	Changes
19-Dec-2012	1	Initial release.
04-Mar-2013	2	– Update schematic and BOM – Add figures for voltage surges dimmer withstanding – Add appendix for heatsink design and schematic with L-C filter
06-Nov-2014	3	Content reworked to improve readability

IMPORTANT NOTICE – PLEASE READ CAREFULLY

STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST's terms and conditions of sale in place at the time of order acknowledgement.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of Purchasers' products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2014 STMicroelectronics – All rights reserved